

Bits & Bots

Anna Gerber

Bits & Bots Sessions


Session	Topic
Tuesday 20 th May, 6 – 8pm	Intro to 3D Design: Design custom robot parts to print on the 3D printers
Tuesday 27 th May, 6 – 8pm	Intro to Electronics: Learn how the electronic parts in the kit work, design our robot circuits
Tuesday 3 rd June, 6 – 8 pm	Intro to Arduino: Write NodeJS programs to read from sensors and control actuators
7 th June, 1 – 5 pm	Intermediate 3D Design: Design more complex robot parts: gears, claws etc
14 th June, 1 – 5 pm	Intermediate Arduino: Develop our robots' locomotion, sensing and responding behaviours
21 st June, 1 – 6 pm	Advanced Bits & Bots: Finalise robot design and assembly, develop advanced robot control programs

Bits & Bots Slides etc

Slides and other materials for the course will be published after each session here:


<https://github.com/AnnaGerber/bits-n-bots>

LED Matrix Pin Out

 

LEDs light up when corresponding column has 5V and row is connected to ground.
Include current limiting resistor for each row

Manually lighting up LEDs

 


- Connect battery 5V and GND to breadboard rails
- Connect ground rail to resistor via a jumper wire and then to a row via another jumper wire
- Connect 5V rail to a column using a jumper wire
- Move the jumper wires to different rows/columns to light a different LED

Shift Registers

- We could connect every row and column pin to pins on an Arduino to control the pattern displayed but this would require a lot of pins
- We will use shift registers to reduce the number of pins required to control the LED Matrix
- How Shift Registers Work:
<https://www.youtube.com/watch?v=Z5iFTBJWz68>

Use this row as ground rail

Use this row as 5V rail

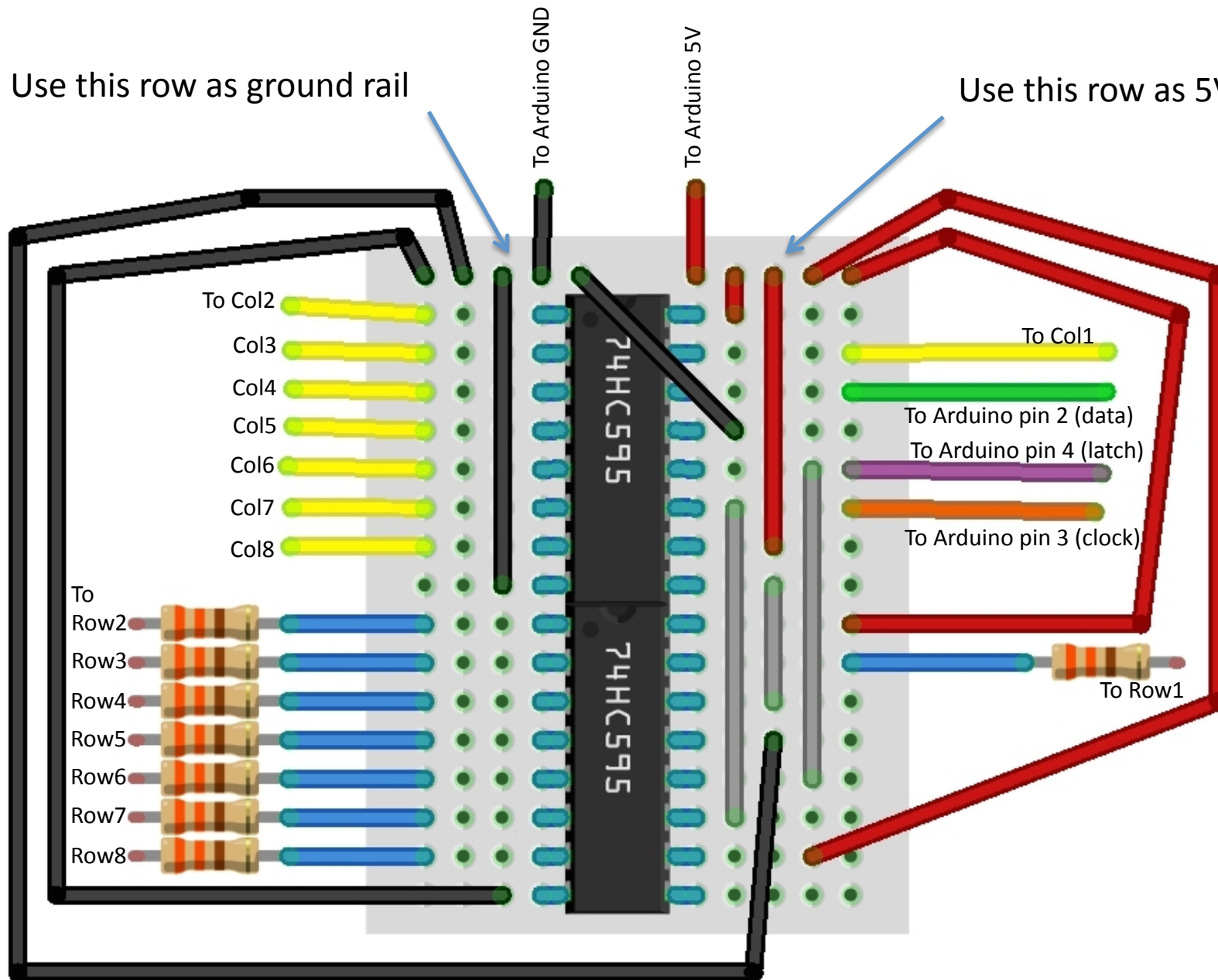

Create a ShiftRegister object

```
var five = require("johnny-five"),
    board, shiftRegister;

board = new five.Board();

board.on("ready", function() {
  shiftRegister = new five.ShiftRegister({
    pins: {
      data: 2,
      clock: 3,
      latch: 4
    }
  });

  this.repl.inject({
    sr: shiftRegister
  });
});
```


Matrix Patterns

- Patterns are represented in binary (each digit represents an LED) and then converted to Hexadecimal values

Pattern	Binary Value	Hex value	Decimal Value
Row or column 8 only	00000001	0x01	1
7 only	00000010	0x02	2
6 only	00000100	0x04	4
5 only	00001000	0x08	8
4 only	00010000	0x10	16
3 only	00100000	0x20	32
2 only	01000000	0x40	64
1 only	10000000	0x80	128

LED on = 1
LED off = 0

Sending patterns

We are shifting an 8 bit pattern in to the first register then a second pattern which will push the first value into the second register.

```
function send2(value, value2) {  
  board.digitalWrite(4, board.io.LOW);  
  board.shiftOut(2, 3, true, (0xff - value));  
  board.shiftOut(2, 3, true, value2);  
  board.digitalWrite(4, board.io.HIGH);  
};  
shiftRegister.send2 = send2;
```

In REPL:

- `sr.send2(0,0) // clear all rows and columns`
- `sr.send2(0xff,0xff) // set all LEDs on`

Creating your own patterns

- Create a pattern for the rows and a pattern for the columns
- Use a calculator to convert the binary number to Hexadecimal or an app e.g.:
<http://www.mathsisfun.com/binary-decimal-hexadecimal-converter.html>

Creating asymmetrical patterns

- We can only send symmetrical patterns directly via the shift register (we could connect to the pins directly or use an alternative controller chip to talk to individual pins)
- To get around this, flash different parts of the pattern in a loop e.g:

```
function flashyX(){  
  board.loop(40, function(){  
    shiftRegister.send2(0x81,0x81);  
    board.wait(10,function(){shiftRegister.send2(0x42,0x42);})  
    board.wait(20,function(){shiftRegister.send2(0x24,0x24);})  
    board.wait(30,function(){shiftRegister.send2(0x18,0x18);})  
  })  
}
```